

EXPLANATIONS

1. (a) The charge $q = \int i dt$.

With $i(t) = 0.02t + 0.01A$,
integrate from $t = 1s$ to $t = 2s$:


$$\int_1^2 (0.02t + 0.01) dt$$

$$q = \left[0.02 \frac{t^2}{2} + 0.01t \right]_1^2$$

$$= 0.01(3) + 0.01(1) = 0.04C$$

2. (a) Resistivity is independent of temperature for wire bound resistors.

3. [2]

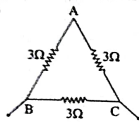

two resistors (3Ω each) are in series, so their total resistance is:

$$R_{\text{series}} = 3\Omega + 3\Omega = 6\Omega$$


Now, the equivalent resistance between B and C is the parallel combination of the 3Ω and 6Ω resistances:

$$\frac{1}{R_{\text{eq}}} = \frac{1}{3\Omega} + \frac{1}{6\Omega}$$

Simplifying:

$$R_{\text{eq}} = 2\Omega$$

4. (b)

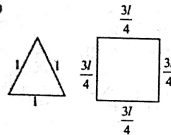

Let resistance corresponding to length l is R .

Then for triangle

$$R_1 = \left(\frac{2R}{3} \right) \times \left(\frac{R}{3} \right) = \left(\frac{2R}{9} \right)$$

For square

$$R_2 = \left(\frac{3}{4} \times \frac{R}{4} \right) \times \frac{R}{4} = \frac{3}{16} R = \left(\frac{3R}{16} \right)$$

$$\frac{R_1}{R_2} = \left(\frac{2R}{9} \right) \times \left(\frac{16}{3R} \right) = \frac{32}{27}$$

5. (b) Given that

$$\text{Current } I = I_0 + \beta t$$

$$I_0 = 20A$$

$$\beta = 3A/s$$

$$I = 20 + 3t$$

$$\frac{dq}{dt} = 20 + 3t$$

$$\int_0^2 dq = \int_0^2 (20 + 3t) dt$$

$$q = \left[20t + \frac{3t^2}{2} \right]_0^2 = 1000C$$

6. (c) Given, $R_{12} = 60\Omega$

$$V = 220V$$

$$I_0 = 2.75A$$

Hence,

$$R_T = \frac{220}{2.75} = 80\Omega$$

Now,

We know that,

$$R = R_0 (1 + \alpha \Delta T)$$

Hence,

$$80 = 60 [1 + 2 \times 10^{-4} (T - 27)]$$

$$T = 1694^\circ C$$

7. (b) For series combination,

$$R_{\text{eq}} = R_1 + R_2$$

$$2R(1 + \alpha_{\text{eq}} \Delta \theta) = R(1 + \alpha_1 \Delta \theta) + R(1 + \alpha_2 \Delta \theta)$$

$$2R(1 + \alpha_{\text{eq}} \Delta \theta) = 2R + (\alpha_1 + \alpha_2) R \Delta \theta$$

$$\alpha_{\text{eq}} = \frac{\alpha_1 + \alpha_2}{2}$$

For parallel combination,

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R(1 + \alpha_{\text{eq}} \Delta \theta)} = \frac{1}{R(1 + \alpha_1 \Delta \theta)} + \frac{1}{R(1 + \alpha_2 \Delta \theta)}$$

$$\frac{2}{1 + \alpha_{\text{eq}} \Delta \theta} = \frac{1}{1 + \alpha_1 \Delta \theta} + \frac{1}{1 + \alpha_2 \Delta \theta}$$

$$\frac{2}{1 + \alpha_{\text{eq}} \Delta \theta} = \frac{1 + \alpha_2 \Delta \theta + 1 + \alpha_1 \Delta \theta}{(1 + \alpha_1 \Delta \theta)(1 + \alpha_2 \Delta \theta)}$$

$$2[(1 + \alpha_1 \Delta \theta)(1 + \alpha_2 \Delta \theta)]$$

$$= [2 + (\alpha_1 + \alpha_2) \Delta \theta][1 + \alpha_{\text{eq}} \Delta \theta]$$

$$2[1 + \alpha_1 \Delta \theta + \alpha_2 \Delta \theta + \alpha_1 \alpha_2 \Delta \theta]$$

$$= 2 + 2\alpha_{\text{eq}} \Delta \theta + (\alpha_1 + \alpha_2) \Delta \theta$$

$$+ \alpha_{\text{eq}} (\alpha_1 + \alpha_2) \Delta \theta^2$$

Neglecting small terms

$$2 + 2(\alpha_1 + \alpha_2) \Delta \theta$$

$$= 2 + 2\alpha_{\text{eq}} \Delta \theta + (\alpha_1 + \alpha_2) \Delta \theta$$

$$(\alpha_1 + \alpha_2) \Delta \theta = 2\alpha_{\text{eq}} \Delta \theta$$

$$\alpha_{\text{eq}} = \frac{\alpha_1 + \alpha_2}{2}$$

$$8. [22] q = \int_1^2 i dt$$

$$\Rightarrow q = (t^3 + t^4) \Big|_1^2 \quad [1 = 3t^3 + 4t^4]$$

$$\therefore q = 22C$$

9. (2) Given $R_{100} = 10\Omega$, $R_0 = 8\Omega$

$$\therefore R_{100} = R_0 (1 + \alpha \Delta T)$$

$$\Rightarrow 10 = 8(1 + \alpha \times 100) \Rightarrow 100\alpha = \frac{1}{4}$$

$$\text{Also, } R_{100} = R_0 (1 + \alpha \Delta T)$$

$$\Rightarrow R_{100} = 8(1 + 400\alpha) = 8(1 + 1) = 16\Omega$$

10. (32)

$$\therefore R = \frac{\rho l}{A} = \frac{\rho l'}{A'} \Rightarrow R \propto \frac{l}{r^2}$$

$$\therefore \frac{R_1}{R_2} = \frac{l_1}{l_2} \times \left(\frac{r_2}{r_1} \right)^2$$

$$\Rightarrow \frac{R_1}{R_2} = \left[\frac{4 \times 10^{-3}}{2 \times 10^{-3}} \right]^2 \Rightarrow R_2 = 32\Omega$$

11. (16)

$$\text{From } R = \frac{\rho l}{A}, R \propto \frac{l}{r^2}$$

On stretching the wire, the length increases, but radius decreases to keep the volume constant, therefore initial volume = final volume

$$\pi r^2 l = \pi r'^2 l'$$

$$l' = 4l$$

$$\frac{R_1}{R_2} = \left(\frac{4l}{l} \right) \times \left(\frac{r_1}{r_2} \right)^2 = 16$$

$$R_1 = 16R \Rightarrow x = 16$$

12. [748]

Resistance of the wire,

$$R = R_0 (1 + \alpha \Delta T)$$

$$\frac{\Delta R}{R_0} = \alpha \Delta T$$

$$\text{Case-I } 0^\circ C \rightarrow 100^\circ C$$

$$\frac{10.2 - 10}{10} = \alpha(100 - 0)$$

$$\text{Case-II } 0^\circ C \rightarrow T^\circ C$$

$$\frac{10.95 - 10}{10} = \alpha(T - 0)$$

$$T = 475 + 273 = 748K$$

13. (1027) We have given the resistance of the element in 50Ω and

$$\alpha = 2.4 \times 10^{-4} C^{-1}$$

$$R = R_0 (1 + \alpha \Delta T)$$

$$62 = 50 [1 + 2.4 \times 10^{-4} \Delta T]$$

$$\Delta T = 1000^\circ C$$

$$\Rightarrow T - 27^\circ = 1000^\circ C$$

$$T = 1027^\circ C$$

14. [300] Volume of wire will remain constant

$$\Rightarrow \pi r_1^2 l_1 = \pi r_2^2 (2l_1)$$

$$r_2 = \frac{r_1}{\sqrt{2}}$$

$$R_2 = \frac{\rho l_2}{\pi r_2^2} = \frac{\rho 2l_1}{\pi \left(\frac{r_1}{\sqrt{2}} \right)^2}$$

$$R_2 = 4 \times \frac{r_1}{\pi r_1^2}$$

$$R_2 = 4R_1$$

$$\% \text{ Change in Resistance} = \frac{\Delta R}{R} \times 100$$

$$= \frac{4R_1 - R_1}{R_1} \times 100 = 300\%$$

15. (c) Volume = constant

$$A l = C$$

$$\therefore \frac{dA}{A} = -\frac{dl}{l}$$

$$\Rightarrow \frac{dA}{A} = -\frac{dl}{l} = -0.4\%$$

$$\text{Now, } R = \frac{\rho l}{A}$$

$$\therefore \frac{\Delta R}{R} \times 100 = \left(\frac{dl}{l} + \frac{dA}{A} \right) \times 100$$

$$= 0.4 + (-0.4) = 0.8\%$$

16. [48]

$$I = A \times j$$

$$= \pi \left(\frac{R^2}{4} \right) j$$

$$= \frac{3\pi R^2}{4} \times j$$

$$= \frac{3\pi \times (4 \times 10^{-3})^2}{4} \times 4 \times 10^6$$

$$= 48\pi$$

17. [12]

Given, Current density $J = 1 \times 10^6 A/m^2$
 $r = 4 \text{ mm} = 4 \times 10^{-3} \text{ m}$

$$r_1 = \frac{r}{2}$$

Formula of current density,

$$J = \frac{I}{A} = \frac{I}{\pi r^2 - \pi (r')^2}$$

$$\therefore I = \left(\pi r^2 - \frac{\pi r'^2}{4} \right) \times J$$

$$= \pi \times \frac{3r^2}{4} \times 1 \times 10^6$$

$$= \pi \times \frac{3}{4} \times 16 \times 10^{-6} \times 10^6$$

$$= 12\pi$$

$$\Rightarrow x = 12$$

18. (a) Using formula, $R_0 = R_1 [1 + \alpha(T - T_0)]$

$$\text{If } T = 10^\circ C \text{ and } R_0 = 2\Omega \text{ then,}$$

$$2 = R_1 [1 + \alpha(10 - T_0)]$$

$$\text{If } T = 30^\circ C \text{ and } R_0 = 3\Omega$$

$$3 = R_1 [1 + \alpha(30 - T_0)]$$

Solving (i) and (ii), we get

$$\alpha = \frac{1}{30} = 0.033$$

19. [144]

We know that, $R = \frac{\rho l}{A}$

$$R = \frac{\rho l}{A} \Rightarrow 1 = \frac{x \times 10^{-3} \times 31.4}{\pi \times (1.2)^2}$$

$$\Rightarrow x = 144$$

20. (a) $R_1 = \rho \frac{l_1}{A_1}$

$$\text{Vol. } V = A l$$

$$A_1 l_1 = A_2 (3l_1)$$

$$\Rightarrow R_2 = \frac{A_1}{A_2}$$

$$\text{So, } R_2 = \rho \left(\frac{3l_1}{A_1/3} \right) = 9\rho \frac{l_1}{A_1}$$

$$\therefore \frac{R_2}{R_1} = 9$$

21. (a) Fact based.

22. (b) Let x be the length of x .

$$\therefore \text{Length of } Y = 1 - x$$

$$\text{And, } R_w = 2Ry$$

$$\Rightarrow \rho \left(\frac{2x}{A/2} \right) = \frac{2\rho(1-x)}{A}$$

$$\Rightarrow x = \frac{1}{3}$$

$$\therefore \frac{L_y}{L_x} = \frac{1/3}{1 - 1/3} = \frac{1}{2}$$

23. (d) $i = \frac{dQ}{dt}$

$$dQ = i dt$$

$$\int_0^t dQ = \int_0^t i dt$$

$$Q = \int_0^t (\alpha_0 t + \beta t^2) dt$$

$$= \left[\alpha_0 \frac{t^2}{2} + \beta \frac{t^3}{3} \right]_{0 \text{ to } 5} - \left[\alpha_0 \frac{t^2}{2} + \beta \frac{t^3}{3} \right]_{0 \text{ to } 0}$$

$$= \left[20 \times \frac{15 \times 15}{2} + 8 \times \frac{15 \times 15 \times 15}{3} \right] - 0$$

$$= 2250 + 9000$$

$$= 11250C$$

24. [5] Given, radius of cylindrical wire, $r = 0.5 \text{ mm}$, conductivity, $\sigma = 5 \times 10^7 \text{ s/m}$, Electric field strength,

$$\vec{E} = 10 \times 10^3 \text{ V/m} = 10^4 \text{ V/m}$$

$$\text{As we know,}$$

$$\therefore J = \sigma E = 5 \times 10^7 \times 10^4 \times \pi \times (0.5 \times 10^{-3})^2$$

$$= 125 \pi \text{ mA} = \pi \times 125 \text{ mA}$$

$$\therefore x = 5$$

25. (a) Relation between current and drift velocity,

$$i = ne A v_d$$

Number of free e- in per-cubic


$$n = \frac{i}{e A v_d}$$

$$= \frac{10}{1.6 \times 10^{-19} \times 5 \times 10^{-4} \times 2 \times 10^{-3}}$$

$$= 625 \times 10^{23}$$

- Current Electricity 333

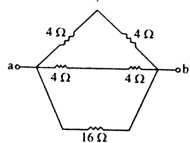54. (b) Using balanced wheat stones bridge (in 4 Ω network)



$$\Rightarrow R_{eq} = \frac{16 \times 4}{16 + 4} = 3.2 \Omega$$


55. (d) Equivalent resistance of circuit $R_{eq} = 3 + 1 + 2 + 4 = 12 \Omega$
Current through the battery is

$$i = \frac{24}{12} = 2 A$$

$$I_4 = \frac{R_4}{R_4 + R_5} \times 2 = \frac{5}{20 + 5} \times 2 = \frac{2}{5} A$$

$$\text{and, } I_5 = 2 - \frac{2}{5} = \frac{8}{5} A$$

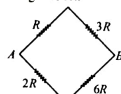
56. (d) As the wheatstone bridge is in balanced condition, no current will flow through the 9R.



$$\Rightarrow \frac{1}{R_{eq}} = \frac{1}{4R} + \frac{1}{8R}$$

$$\Rightarrow R_{eq} = \frac{8R}{3}$$


57. (d)

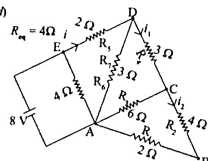


$$i = \frac{8}{3} = 2.4; I_1 = \frac{2 \times 3}{3 + 6} = \frac{2}{3} A$$

$$I_2 = \frac{2/3}{2} = \frac{1}{3} A$$

58. [10]

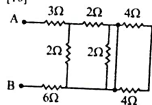

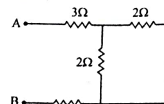Both 4 Ω resistance gets short due to the conducting wire parallel to 2 Ω .
Therefore 4 Ω resistors that have no current.



$$R_{eq} = 3 + (2 \parallel 6) = 3 + 1 + 6$$

$$\Rightarrow R_{eq} = 10 \Omega$$

$$59. [2] \frac{2}{3} = \frac{x+1}{x}$$

$$\Rightarrow \frac{2}{3} = \frac{x}{x+1} \Rightarrow x = 0.5 = \frac{1}{2}$$

60. [100] Series combination gives maximum resistance whereas parallel combination gives minimum resistance.

$$R_{max} = 10 R, R_{min} = \frac{R}{10}$$

$$\therefore \frac{R_{max}}{R_{min}} = \frac{10R}{R/10} = 100$$

61. (b) $R = R_1 + R_2$

$$\Rightarrow \frac{1}{\sigma A} = \frac{1}{\sigma_1 A} + \frac{1}{\sigma_2 A} \Rightarrow \sigma = \frac{2\sigma_1\sigma_2}{\sigma_1 + \sigma_2}$$

62. [4] Formula of resistance, $R = \frac{\rho l}{A}$
Equivalent resistance of eight wire in parallel is $R/8$


According to question,

$$R = \frac{\rho l}{A} \Rightarrow R \propto \frac{l}{d^2}$$

$$\frac{R_1}{R_2} = \frac{l_1}{l_2} \cdot \frac{d_2^2}{d_1^2}$$

$$\frac{R}{R} = \frac{1}{3} \cdot \frac{d_2^2}{d^2} \Rightarrow d_2 = 4d$$

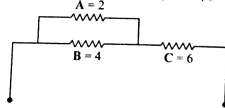63. (b) It is given that, $A = 2 \Omega, B = 4 \Omega, C = 6 \Omega$.



From the diagram given above,

$$R_{eq} = \frac{2 \times 4}{2 + 4} + 6 = \frac{8}{6} + 6 = \frac{4}{3} + 6$$

$$\therefore R_{eq} = \frac{22}{3} \Omega$$

64. (a) Arrangement of the resistors is equivalent to wheat stone bridge. Therefore equivalent resistance of the circuit.

$$R_{eq} = \frac{4 \times 4}{4 + 4} + \frac{4 \times 4}{4 + 4} = 4 \Omega$$

From ohm's law

$$I = \frac{V}{R} = \frac{40}{4} = 10 A$$

65. (a) Statement-I

$$80 = \frac{\rho l}{A}$$

$$R' = \frac{\rho l}{A} = \frac{80}{4} = 20 \Omega$$

$$\text{So, } R_{eq} = \frac{R'}{4} = \frac{20}{4} = 5 \Omega$$

Statement-II





$$\frac{R_1}{R_2} = \frac{l_1^2}{l_2^2} \Rightarrow \frac{3R}{2R} = \frac{l_1^2}{l_2^2}$$

66. (a) The circuit is balanced wheatstone bridge. So there is no current in 5 Ω resistor.

$$\Rightarrow R_{eq} = \frac{6 \times 12}{6 + 12} + 2 = 6 \Omega$$

$$\Rightarrow I = \frac{V}{R} = \frac{6}{6} = 1 A$$

67. [8]

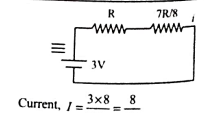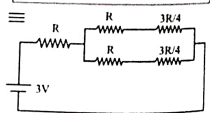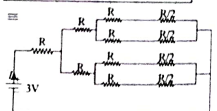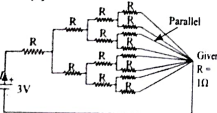

Current, $I = \frac{3 \times 8}{15R} = \frac{8}{5R}$
On comparing above result with $I = \frac{\rho l}{A}$, we get $a = 8$

68. [2] Equivalent resistance of parallel combination of three resistors = 3 ohm, $I = 6/3 = 2 A$

69. [3] Equivalent resistance of the circuit

$$R_{eq} = \frac{ma}{3} + \frac{a}{2m}$$

$$\frac{dR_{eq}}{dm} = 0 \Rightarrow \frac{a}{3} - \frac{a}{2m^2} = 0$$

$$m^2 = \frac{3}{2} \Rightarrow m = \sqrt{\frac{3}{2}}$$

$$x = 3$$


70. (c) Using hit and trial method, from option (c) we get,

$$R_{eq} = \frac{2 \times 4}{2 + 4} + 6 + 8 = \frac{46}{3} \Omega$$

71. (b) As, 5 Ω is connected across conductor

$$\text{so we can remove it. } R_{eq} = \frac{3 \times \frac{3}{2}}{\frac{3}{2} + 2} = 1 \Omega$$

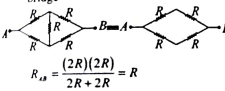72. (b) Given circuit can be re-drawn and it becomes case of balanced Wheatstone bridge



$$73. (a) R_1 = \rho_1 \frac{l}{A}, R_2 = \rho_2 \frac{l}{A}$$

Equivalent resistance in parallel form.

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{A}{l} \left[\frac{1}{\rho_1} + \frac{1}{\rho_2} \right]$$

$$= \frac{3 \times 10^{-4}}{4} \left[\frac{1}{1.7 \times 10^{-8}} + \frac{1}{2.6 \times 10^{-8}} \right]$$

$$= 12 \times 10^{-4} \left[\frac{10}{17} + \frac{10}{26} \right]$$

$$R = 0.858 \times 10^{-1} \Omega$$

$$74. (d) \text{ Formula of resistance, } R = \frac{\rho l}{A}$$

$$\rho_1 = 12 \mu \text{ cm}$$

$$\rho_2 = 51 \mu \text{ cm}$$

$$\text{Equivalent resistance, } \frac{R_1 R_2}{R_1 + R_2} = 3$$

$$\left(\frac{\rho_1 l}{A} \right) \left(\frac{\rho_2 l}{A} \right) = 3$$

$$\left(\frac{\rho_1 l}{A} \right) + \left(\frac{\rho_2 l}{A} \right) = 3$$

$$l = \frac{3A(\rho_1 + \rho_2)}{\rho_1 \rho_2}$$

$$3 \times \left[\frac{\pi}{4} \times (2 \times 10^{-3})^2 \right] = \frac{12 \times 10^{-6} \times 10^{-2} \times 51 \times 10^{-6} \times 10^{-2}}{97 \text{ m}}$$

$$75. (b) \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{4} + \frac{1}{4}$$

$$\Rightarrow R_{eq} = 2$$


$$\frac{\Delta R_{eq}}{R_{eq}^2} = \frac{\Delta R_1}{R_1^2} + \frac{\Delta R_2}{R_2^2}$$

$$\frac{\Delta R_{eq}}{R_{eq}^2} = \frac{0.8}{4} + \frac{0.4}{16} + \frac{1.2}{16}$$

$$\text{So, } \Delta R_{eq} = 0.3$$


$$\therefore R_{eq} = (2 \pm 0.3) \Omega$$

76. [9] When switch is open,

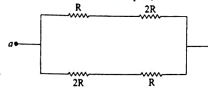

$$R_{eq} = \frac{3R}{2}$$

When switch is closed,

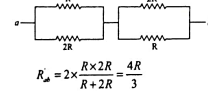

$$R_{eq} = 2 \times \frac{R \times 2R}{R + 2R} = \frac{4R}{3}$$

$$\frac{R_{eq}}{R_{eq}'} = \frac{3R/2}{4R/3} = \frac{9}{8} \Rightarrow x = 9$$



77. [6] Equivalent resistance, $R_{eq} = 6 \Omega$
Current through the battery,

$$i = \frac{12V}{6\Omega} = 2 A$$

Voltage across, 15 Ω resistance, $V(15 \Omega)$

$$= 6 V$$

78. [3]

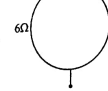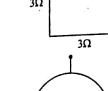

$$R_{eq} = \frac{6 \times 6}{12} = 3$$

79. [3] $R_{eq} = 5 + 1 + 1 = 7 \Omega$

$$\therefore I = \frac{V_{eq}}{R_{eq}} = \frac{21}{7 \times 10^3} = 3 \text{ mA}$$

80. [70]

$$R_{eq} = 10 + \frac{50 \times 20}{50 + 20} = \frac{170}{7} \Omega$$

$$\Rightarrow i = \frac{170}{\frac{170}{7}} = 7 A$$

$$\Rightarrow x = 10 \times 7 = 70 V$$

81. [2] Using KCL at P, $i_1 + i_2 = 6$... (i)

and using KVL in closed circuit PQRP.

Solving above equations, we get, $i_1 = 2 A$.

82. [20]

In series combination, $R_{eq} = nR = 10n$

$$\Rightarrow I_{eq} = \frac{20}{10 + 10n} = \frac{2}{1 + n}$$

In parallel combination, $R_{eq} = \frac{10}{n}$

$$\Rightarrow I_p = \frac{20}{\frac{10}{n} + 10} = \frac{2n}{1 + n}$$

According to the question,

$$\Rightarrow \frac{I_p}{I_{eq}} = 20 = \frac{2n/1 + n}{2/1 + n} \Rightarrow n = 20$$

83. [4] In parallel combination,

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

$$\Rightarrow \frac{\rho l}{2A} = \frac{\rho_1 l}{A} \times \frac{\rho_2 l}{A} \left(\because R = \rho \frac{l}{A} \right)$$

$$\Rightarrow \frac{\rho}{2} = \frac{6 \times 3}{2} = 2$$

$$\Rightarrow \rho = 2 \times 2 = 4 \Omega - \text{cm}$$

84. [4] $s = np$

$$R_1 + R_2 = n \left[\frac{R_1 R_2}{R_1 + R_2} \right]$$

$$\Rightarrow R_1^2 + R_2^2 + 2R_1 R_2 = n R_1 R_2$$

$$\Rightarrow R_1^2 + (2 - n) R_1 R_2 + R_2^2 = 0$$

For real roots, $b^2 - 4ac \geq 0$


$$[(2 - n) R_1]^2 - 4 \times 1 \times R_2^2 \geq 0$$

$$\Rightarrow (2 - 4)^2 R_1^2 \geq 4 R_2^2 \Rightarrow 2 - n \geq 2$$

$$\Rightarrow 2 - n \geq 2 \Rightarrow n \geq 4$$

So, minimum value for $n = 4$

85. [10]

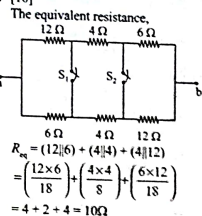


86. (c) Resistance in parallel

$$= \frac{R_1 R_2}{R_1 + R_2} = \frac{1}{2}\Omega$$


Now, resistance in series R'

$$= \frac{1}{2} + 2 = 2.5\Omega$$

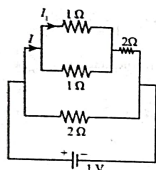

Current through upper branch


$$I = \frac{1}{2.5} = 0.4A$$

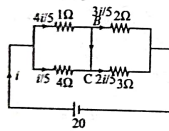Current through 1Ω (I_1) = $\frac{I}{2} = 0.2A$ 87. (b) $R_p = \frac{4}{5} + \frac{6}{5} = 2\Omega$ 

$$i = \frac{20}{2} = 10A$$

$$I = \frac{4i}{5} - \frac{3i}{5} = +\frac{i}{5} = 2A$$

88. [10]

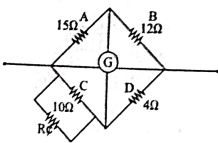


Wheatstone bridge balance conditions

$$\frac{A}{B} = \frac{C}{D}$$

$$\Rightarrow \frac{10 R'}{10 + R'} \times 12 = 15 \times 4$$

On solving
 $R' = 10\Omega$

89. (b)

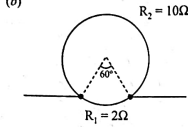


$$\Rightarrow R = \frac{\rho L}{A} = \frac{\rho L^2}{A^2} \quad R \propto L^2$$

 $R = 12\Omega$ (new resistance of wire)

$$R_1 = 2\Omega, R_2 = 10\Omega$$


$$R_{eq} = \frac{10 \times 2}{10 + 2} = \frac{2}{3}\Omega$$

90. (a)

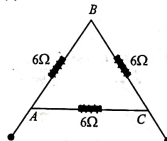

$$\text{So, } R_{AC} = \frac{12 \times 6}{18} = 4\Omega$$

91. (c)

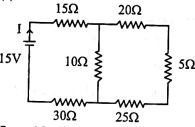


$$R_{eq} = 15 + \left(\frac{20 + 5 + 25}{10} \right) \parallel 10 + 30$$

$$R_{eq} = 15 + \frac{25}{3} + 30 = \frac{160}{3}$$

$$\text{Current, } I = \frac{E}{R_{eq}} = \frac{15}{\left(\frac{160}{3} \right)} = \frac{9}{32} \text{ amp}$$

92. (a)

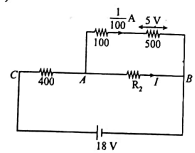

$$V_{AB} = \left(\frac{1}{100} \right) 600 = 6 \text{ volt}$$


$$\Rightarrow V_{AC} = 18V - 6V = 12 \text{ volt}$$

$$I_{AC} = \frac{12}{400} = \frac{3}{100} \Rightarrow I = I_{AC} = \frac{1}{100}$$

$$\Rightarrow I = \frac{3}{100} = \frac{1}{2}$$

$$\Rightarrow R_2 = \frac{V_{AB}}{I} = \frac{6 \times 100}{2} = 300\Omega$$

93. (b)

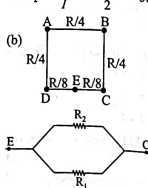

$$R_1 = \frac{R}{8}, R_2 = \frac{R}{8} + \frac{R}{4} + \frac{R}{4} + \frac{R}{4} + \frac{R}{8}$$

$$\frac{1}{R_{EC}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_{EC}} = \frac{1}{8} + \frac{8}{R}$$

$$R_{EC} = \frac{7R}{8 + 56} = \frac{7R}{64}$$

94. (c) Resistance of each bulb is:

$$R = \frac{V_{total}^2}{P} \quad (\text{from } P = \frac{V_{total}^2}{R} \text{ when alone})$$

Total resistance, when resistors are connected in series:

$$R_s = nR = n \cdot \frac{V_{total}^2}{P}$$

$$\text{Total power: } P_s = \frac{V_{total}^2}{R_s} = \frac{V_{total}^2}{n \cdot \frac{V_{total}^2}{P}} = \frac{P}{n}$$

95. (c) Given: Voltage $V = 100V$, Current $I = 1A$.

So, total input power.

$$P_{in} = V \times I = 100W$$

Efficiency is: $\eta = \frac{P_{out}}{P_{in}} = 0.916$ Thus, useful output power: $P_{out} = 0.916 \times 100 = 91.6W$ Power lost: $\text{Loss} = P_{in} - P_{out} = 100 - 91.6 = 8.4W = 2 \text{ cal/s}$ 96. (d) $\frac{V^2}{R} = W$

When the wire is cut into two halves

$$\frac{V^2}{\left(\frac{R}{2} \right)} = W'$$

From (i) & (ii), we get

$$W' = 4W$$

97. (c) Power, $P = i^2 R$

$$P_{in} = i_{in}^2 R$$

$$P_{out} = (0.8 i_{in})^2 R$$

% change in power =

$$= \frac{P_{final} - P_{initial}}{P_{initial}} \times 100$$

$$= (0.64 - 1) \times 100 = -36\%$$

98. [3] Equivalent Resistance,

$$R_{eq} = \frac{4}{3}\Omega$$

$$\text{We know, } P = \frac{V^2}{R} = \frac{4}{4/3} = 3\Omega$$

99. (a) Resistance,

$$R = \frac{V^2}{P} = \frac{(200)^2}{50} = \frac{40000}{50}$$

$$R = 800\Omega$$

Power dissipated

$$P = \left(\frac{V_{applied}}{R} \right)^2 = \frac{(100)^2}{800} = 12.5 \text{ watt}$$

100. (b) The current through 5Ω resistor is i_1 and 10Ω resistor is i_2

$$\frac{i_1}{i_2} = \frac{10}{5} = \frac{2}{1}$$

$$\frac{P_1}{P_2} = \frac{i_1^2 R_1}{i_2^2 R_2} = \left(\frac{2}{1} \right)^2 \times \frac{5}{10} = \frac{2}{1}$$

101. (c) Resistance of the material, $R = \frac{\rho L}{A}$

$$\text{Now, } P = \frac{V^2}{R} \Rightarrow P \propto \frac{1}{L}$$

$$\Rightarrow \frac{P_1}{P_2} = \frac{L_2}{L_1} = \frac{15}{20} = \frac{3}{4}$$

$$\therefore L_2 = \frac{3}{4} L_1$$


102. [5] Resistance of the heater,

$$R_{heater} = \frac{V^2}{P} = \frac{(100)^2}{1000} = 10\Omega$$

For heater, $P_{heater} = \frac{V^2}{R} \Rightarrow V = \sqrt{PR}$

$$V = \sqrt{62.5 \times 10} \Rightarrow V = 25V$$

... (ii)

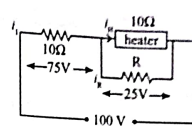

$$I_1 = \frac{75}{10} = 7.5A, I_2 = \frac{25}{10} = 2.5A$$

$$I_3 = I_1 - I_2 = 5$$

Using ohm's law, $V = IR$

$$\therefore R = \frac{25}{5} = 5\Omega$$

103. (b) $H = FRt = 42R \times 10 = 160R$

$$H = (I^2) R t = 162R \times 10 = 2560R = 16H$$

104. (d) The formula of power $P = FR_{eq}$ $\Rightarrow P \propto Req$

$$R_A = \frac{3R}{2}, R_B = \frac{2R}{3}, R_C = \frac{R}{3}, R_D = 3R$$

105. (a) Heat energy produced in a resistor R connected to potential difference V is

$$H = \frac{V^2}{R} \times t$$

$$H = \frac{V^2}{R} \times t$$

$$\Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = 3:1$$

As the resistors are connected in parallel

$$H = \frac{V^2}{R} \times t$$

106. (a) Parallel combination, $Req = \frac{R}{2}$

$$H = \frac{V^2}{R} \times t$$

$$\Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = 3:1$$

$$\Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = 3:1$$

$$\Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = 3:1$$

$$\Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = 3:1$$

$$\Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = 3:1$$

$$\Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = 3:1$$

$$\Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = 3:1$$

$$\Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = 3:1$$

$$\Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = 3:1$$

$$\Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = 3:1$$

$$\Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = 3:1$$

$$\Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = 3:1$$

$$\Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = 3:1$$

$$\Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = 3:1$$

$$\Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = 3:1$$

$$\Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = 3:1$$

$$\Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = 3:1$$

$$\Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = 3:1$$

$$\Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = 3:1$$

$$\Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = 3:1$$

$$\Rightarrow \frac{H_1}{H_2} = \frac{R_2}{R_1} = 3:1$$

108. [14]

$$\frac{V_1}{V_2} = \frac{R_1}{R_2} = \frac{P_1}{P_2} = \frac{60}{3} = \frac{20}{1}$$

$$V_1 = \frac{3}{8} \times 220 = 3 \times 27.5 = 82.5V$$

$$\therefore P_1 = \left(\frac{V_1}{V_2} \right)^2 P_2 = \left(\frac{330}{220} \right)^2 \times 100 = 14W$$

109. [450]

$$H = i^2 R t$$

$$300 = 2^2 \times R \times 15$$

$$\Rightarrow R = 300 / 60 = 5\Omega$$

Now, for $i = 3A, t = 10s, R = 5\Omega$

$$H = 3^2 \times 5 \times 10 = 450J$$

110. (a) $R_{eq} = \frac{V^2}{P_{max}} = \frac{100 \times 100}{500} = 20\Omega$

$$I = \frac{V_{max}}{R_{max} + R} = \frac{200}{20 + R}$$


$$\Rightarrow \left(\frac{200}{20 + R} \right)^2 \times 20 = 500$$

$$\Rightarrow (20 + R)^2 = \frac{200 \times 200 \times 20}{500} = 1600$$

$$\Rightarrow 20 + R = 40$$

$$\therefore R = 20\Omega$$

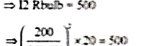111. (a) Equivalent resistance of the circuit.



$$= 0.6\Omega + \frac{12}{3} = 0.6\Omega + 4 = 4.6\Omega$$

$$= 0.6\Omega + \frac{(144/14)\Omega}{14}$$

$$= 0.6\Omega + 1.6\Omega = 2.2\Omega$$

Power dissipated in the circuit

$$P = \frac{V^2}{R_{eq}} = \frac{(2.2V)^2}{2.2\Omega} = 2.2W$$

$$\Delta U = \Delta Q - \Delta W$$

$$\frac{\Delta U}{\Delta t} = \frac{\Delta Q}{\Delta t} - \frac{\Delta W}{\Delta t} = \frac{6000}{60} - 90 = 101/5$$

$$t = \frac{\Delta U}{10} = \frac{2.5 \times 10^3}{10} = 2.5 \times 10^2 \text{ seconds}$$

113. (a) Using Joule's law of heating, heat generated in the resistance $H = i^2 R t$
 $H_1 = 500 = (5)^2 R (20)$

$$H_2 = (3)^2 R (20) \Rightarrow H_2 = H_1 \times \left(\frac{3}{5}\right)^2$$

$$= 500 \times \frac{9}{25} = 2000 \text{ J}$$

114. [3840] $E = \rho R l$
 $\Rightarrow 192 = 4^2 R (1)$
 $\Rightarrow R = 12 \Omega$
 As current is doubled and time = 5s
 So, energy dissipated in this case $E = 3840 \text{ J}$

115. [4] In first condition $R_1 = 36 \Omega$

In second condition $R_2 = 18 \Omega$

$$P_1 = \frac{V^2}{R_1} = \frac{(240)^2}{36}$$

$$P_2 = \frac{V^2}{R_2} = \frac{(240)^2}{18} = \frac{(240)^2}{18}$$

$$P_2 = \frac{(240)^2}{9}$$

$$\frac{P_2}{P_1} = \frac{(240)^2 / 9}{(240)^2 / 36} = \frac{1}{4} \quad x = 4$$

116. [2500] Energy dissipated by a resistor $H = i^2 R t$

$$R = \frac{10 \times 10^{-3}}{(2 \times 10^{-3})^2 \times 1} = 2500 \Omega$$

Hence, the resistance is 2500 W

117. [50] Given, $P = 20 \text{ W}$, Supply voltage, $V_s = 200 \text{ V}$
 Resistance of electric Bulb,

$$R_B = \frac{V^2}{P} = \frac{(200)^2}{20} = 50 \Omega$$

Formula of power, $P = F(R_B)$

$$= \left(\frac{V}{R + R_B}\right)^2 R_B$$

$$= \left(\frac{200}{R + 50}\right)^2 \times 50 = 200$$

$$R = 50 \Omega$$

118. (b) Total power consumed (P) is $(15 \times 45) + (15 \times 100) + (15 \times 10) + (2 \times 1000) = 4325 \text{ W}$
 So, current (I)

$$\text{Power consumed} = \frac{4325}{220} = 19.66 \text{ A}$$

$$\text{Voltage supplied} = 220$$

Hence, answer is 20 Amp.

119. (c) Power in external $R = \left(\frac{E}{r + R}\right)^2 R$

This power is maximum, when $R = r$

$$r = \int_0^{\infty} P \frac{dx}{2\pi x l}$$

$$r = \frac{\rho}{2\pi l} \ln \frac{b}{a}$$

120. (a) $P R = 0.5$

$$i R = 2.5$$

$$\Rightarrow i = 0.2 \text{ A and}$$

$$R = 12.5 \Omega$$

$$V = E - i r$$

$$2.5 = 3.0 - 0.2 r$$

$$\Rightarrow r = 2.5 \Omega$$

Power dissipated in internal resistance

$$P_r = \frac{P_R}{R/r} = \frac{0.5}{5} = 0.1 \text{ W} = i^2 r = 0.1 \text{ W}$$

121. (a) $R_{eq} = (4R/3) + R + (6R + 12R) + R$

$$R_{eq} = 8R$$


$$\therefore p = \frac{V^2}{R_{eq}} = \frac{(16)^2}{8R} = 4$$

$$\therefore R = 8 \Omega$$

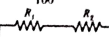122. (a) Resistance, $R = \frac{V^2}{P}$

$$\Rightarrow R_1 = \frac{(200)^2}{25} = 1936 \Omega$$

$$R_2 = \frac{(200)^2}{100} = 484 \Omega$$




$$i = \frac{220}{R_1 + R_2} = \frac{1}{11} \text{ A} = 0.09 \text{ A}$$


Dissipated powers,

$$P_1 = i^2 R_1 = (0.09)^2 \times 1936 = 16 \text{ W}$$
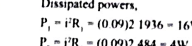
$$P_2 = i^2 R_2 = (0.09)^2 \times 484 = 4 \text{ W}$$



$$123. (d)$$

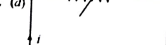

Internal resistance = r

External resistance = R

For maximum power delivered by cell
 Internal resistance = External resistance

$$\Rightarrow r = R$$

124. (a) $R = \frac{P}{I^2} = \frac{4.4}{(1.1 \times 10^3)^2} = 1.1 \times 10^{-6} \Omega$

$$P' = \frac{V^2}{R} = \frac{(11)^2}{1.1 \times 10^{-6}} = 11 \times 10^3 \text{ W}$$

125. (b) When resistances are connected in parallel,

$$P_1 = \frac{P_1 P_2}{P_1 + P_2} = 60$$

$$\therefore P_1 = P_2$$

$$\therefore P_1 = P_2 = 120 \text{ W}$$

So total consumed power

$$P' = P_1 + P_2 = 120 + 120 = 240 \text{ W}$$

126. (b) $Q = \Delta T + m L$

$$Q = m c \Delta T + m L$$

$$P = \frac{V^2}{R}$$

$$4200 \times 80 + 2260 \times 10^3 = \frac{(200)^2}{20} \times t$$

$$\Rightarrow t = 1298 \text{ sec} = 21.6 \text{ min}$$

$$t = 22 \text{ min}$$

127. (a) By colour coding,

$$R = 50 \times 10^3 \Omega$$

$$F R = P$$

The maximum current which can be passed through the resistor

$$I = \sqrt{\frac{P}{R}} = 20 \text{ mA}$$

128. [5] The equivalent resistance

$$R_{eq} = R_1 + \frac{R_2 R_3}{R_2 + R_3}$$

$$\text{where } R_1 = 150 \Omega, R_2 = 240 \Omega,$$

and $R_3 = 10 \Omega$. Thus,

$$R_{eq} = 150 \Omega + \frac{240 \times 10}{240 + 10} = 150 \Omega + 9.6 = 160 \Omega$$

$$\frac{V}{R_{eq}} = \frac{240}{160} = 1.5 \text{ A} \times 0.125 = 0.1875 \text{ A}$$

$$= 0.005 \text{ A} = 5 \text{ mA}$$



129. [4] The total current $I = \frac{V}{R_{eq}} = \frac{20}{160} = 0.125 \text{ A}$

The ammeter current

$$I_2 = I_1 \times \frac{9.6}{240} = 0.125 \times \frac{9.6}{240}$$

$$= 0.005 \text{ A} = 5 \text{ mA}$$


130. [4] The equivalent resistance

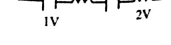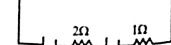

$$e_{eq} = 3$$

$$R_{eq} = 9 \Omega$$

$$i = \frac{3}{6} = \frac{1}{2}$$

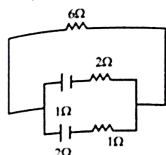

$$e_1 + e_2$$

$$e_1 = \frac{V_1}{R_1} = \frac{4}{3}$$

$$e_2 = \frac{V_2}{R_2} = \frac{2}{3}$$

$$e_{eq} = \frac{2 \times 1}{3} + 6 = \frac{20}{3}$$




130. (d) The equivalent EMF of two non-ideal batteries connected in parallel is given by:

$$E_{eq} = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2}$$

where E_1, E_2 are the EMFs of the two batteries and r_1, r_2 are their internal resistances

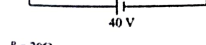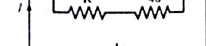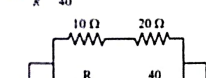131. [2] This balanced is wheatstone bridge.



$$\text{So, } \frac{10}{R} = \frac{20}{40}$$



$$R = 20 \Omega$$

$$I = \frac{40}{20} = 2 \text{ A}$$

132. [6]

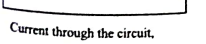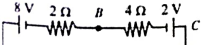

Current through the circuit,


$$I = \frac{8 - 2}{2 + 4} = 1 \text{ A}$$

Applying Kirchhoff from C to B

$$V_C - 2 - 4 \times 1 = V_B$$

$$V_C - V_B = 6 \text{ V}$$

133. (1)

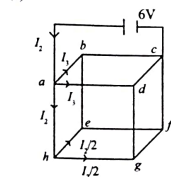

From symmetry, current through e - b & g - d = 0

$$\therefore R_{eq} = \frac{3}{4} \times R = \frac{3}{2} \Omega$$

$$\text{Current through battery} = \frac{6 \times 2}{3} = 4 \text{ A}$$

$$\text{and } I_2 = \frac{4}{8} \times 2 = 1 \text{ A}$$

$$\therefore \Delta V \text{ across e-f}$$

$$= I_2 \times R = \frac{1}{2} \times 2 = 1 \text{ V}$$

134. (a)


Using ohm's law, $V = IR$

$$\text{Current in the circuit, } i = \frac{3}{1 + 2} = 1 \text{ A}$$

$$V = E - i r$$

$$= 3 - 1 \times 1 = 2 \text{ V}$$

135. [25]

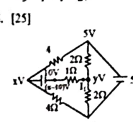

Applying KCL,

$$y - 5 + \frac{y - 0}{2} + \frac{y - x + 10}{1} = 0$$

$$y - 5 + y + 2y - 2x + 20 = 0$$

$$4y - 2x + 15 = 0 \quad \dots(i)$$

$$\frac{x - 5}{4} + \frac{x - 0}{4} + \frac{x - 10 - y}{1} = 0$$

$$x - 5 + x + 4x - 40 - 4y = 0$$

$$6x - 4y - 45 = 0 \quad \dots(ii)$$

From equation (i) and (ii), we get

$$x = \frac{15}{2} \text{ and } 4y - 15 + 15 = 0$$

$$y = 0$$

$$\therefore i = \frac{y - x + 10}{1} = \frac{0 - 7.5 + 10}{1} = 2.5 \text{ A}$$

$$\Rightarrow i = 2.5 \text{ A} = \frac{n}{10} \Rightarrow n = 25$$

$$\therefore i = 2.5 \text{ A} = \frac{n}{10} \Rightarrow n = 25$$

$$\therefore i = 2.5 \text{ A} = \frac{n}{10} \Rightarrow n = 25$$


$$\therefore i = 2.5 \text{ A} = \frac{n}{10} \Rightarrow n = 25$$

$$y = 0$$

$$\therefore i = \frac{y - x + 10}{1} = \frac{0 - 7.5 + 10}{1}$$

$$\Rightarrow i = 2.5 \text{ A} = \frac{n}{10} \Rightarrow n = 25$$

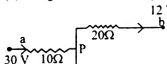136. (a) Using Kirchhoff's law at point P



$$\frac{P - 30}{10} + \frac{P - 12}{20} + \frac{P - 2}{30} = 0$$

$$P \left(\frac{1}{10} + \frac{1}{20} + \frac{1}{30} \right) = \frac{30}{10} + \frac{12}{20} + \frac{2}{30}$$

$$P \left(\frac{6 + 3 + 2}{60} \right) = \frac{108 + 36 + 4}{60} = 208$$

$$\therefore i_{20\Omega} = \frac{x - 12}{20} = \frac{20 - 12}{20} = 0.4 \text{ A}$$

$$\therefore i_{20\Omega} = \frac{x - 12}{20} = \frac{20 - 12}{20} = 0.4 \text{ A}$$

$$\therefore i_{20\Omega} = \frac{x - 12}{20} = \frac{20 - 12}{20} = 0.4 \text{ A}$$

$$\therefore i_{20\Omega} = \frac{x - 12}{20} = \frac{20 - 12}{20} = 0.4 \text{ A}$$

$$\therefore i_{20\Omega} = \frac{x - 12}{20} = \frac{20 - 12}{20} = 0.4 \text{ A}$$

$$\therefore i_{20\Omega} = \frac{x - 12}{20} = \frac{20 - 12}{20} = 0.4 \text{ A}$$

$$\therefore i_{20\Omega} = \frac{x - 12}{20} = \frac{20 - 12}{20} = 0.4 \text{ A}$$

$$\therefore i_{20\Omega} = \frac{x - 12}{20} = \frac{20 - 12}{20} = 0.4 \text{ A}$$

$$\therefore i_{20\Omega} = \frac{x - 12}{20} = \frac{20 - 12}{20} = 0.4 \text{ A}$$

$$\therefore i_{20\Omega} = \frac{x - 12}{20} = \frac{20 - 12}{20} = 0.4 \text{ A}$$

$$\therefore i_{20\Omega} = \frac{x - 12}{20} = \frac{20 - 12}{20} = 0.4 \text{ A}$$

$$\therefore i_{20\Omega} = \frac{x - 12}{20} = \frac{20 - 12}{20} = 0.4 \text{ A}$$

$$\therefore i_{20\Omega} = \frac{x - 12}{20} = \frac{20 - 12}{20} = 0.4 \text{ A}$$

$$\therefore i_{20\Omega} = \frac{x - 12}{20} = \frac{20 - 12}{20} = 0.4 \text{ A}$$

$$\therefore i_{20\Omega} = \frac{x - 12}{20} = \frac{20 - 12}{20} = 0.4 \text{ A}$$

$$\therefore i_{20\Omega} = \frac{x - 12}{20} = \frac{20 - 12}{20} = 0.4 \text{ A}$$

$$\therefore i_{20\Omega} = \frac{x - 12}{20} = \frac{20 - 12}{20} = 0.4 \text{ A}$$

$$\therefore i_{20\Omega} = \frac{x - 12}{20} = \frac{20 - 12}{20} = 0.4 \text{ A}$$

$$\therefore i_{20\Omega} = \frac{x - 12}{20} = \frac{20 - 12}{20} = 0.4 \text{ A}$$

$$\therefore i_{20\Omega} = \frac{x - 12}{20} = \frac{20 - 12}{20} = 0.4 \text{ A}$$

$$\therefore i_{20\Omega} = \frac{x - 12}{20} = \frac{20 - 12}{20} = 0.4 \text{ A}$$

$$\therefore i_{20\Omega} = \frac{x - 12}{20} = \frac{20 - 12}{20} = 0.4 \text{ A}$$

138. (a) We have,


$$E_1 = E_2 = E$$

$$\therefore I = \frac{V_{\text{net}}}{R_{\text{net}}} = \frac{2E}{R + r_1 + r_2}$$

Potential drop across second cell is

$$V_A - E_2 + Ir_2 = V_B$$

$$V_A - V_B = E_2 - Ir_2 = 2$$

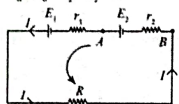


According to question $V_A - V_B = 0$

$$E_2 - Ir_2 = 0$$

$$\Rightarrow R + r_1 - 2r_2 = 0$$


$$\Rightarrow R = r_2 - r_1$$

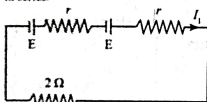139. (a) Case I: when the cells are connected in series.



$$I_1 = \frac{2E}{2r+2} \quad \dots(i)$$

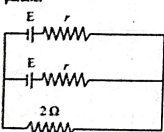Case II: when the cells are connected in parallel



$$I_2 = \frac{E}{\frac{r}{2} + 2} = \frac{2E}{r+4} \quad \dots(ii)$$

According to the question, $I_1 = I_2$
From (i) and (ii),

$$\frac{2E}{2r+2} = \frac{2E}{r+4} \Rightarrow \frac{2}{2r+2} = \frac{2}{r+4}$$

$$\Rightarrow 2r+2 = r+4$$

$$\Rightarrow r = 2 \Omega$$

140. (d) Equivalent resistance of the circuit.

$$R_{\text{eq}} = 5 + \frac{10 \times 5}{10+5} = \frac{55}{3} \text{ k}\Omega$$

From Ohm's law,

$$V_{AB} = R_{\text{eq}} I$$

$$= \left(\frac{55}{3} \times 10^3 \right) \times \left(15 \times 10^{-3} \right) = 275 \text{ V}$$

141. (d) $R_{\text{eq}} = r_1 + r_2 + R$

$$\therefore I = \frac{2E}{r_1 + r_2 + R}$$

According to the question,

$$-(V_A - V_B) = E - Ir_2$$

$$0 = E - Ir_2$$

$$E = Ir_2$$

$$E = \frac{2E}{r_1 + r_2 + R} r_2$$

$$r_1 + r_2 + R = 2r_2$$


$$\therefore R = r_2 - r_1$$

142. [4] From Nodal analysis,

$$\frac{V_2 - 2}{1 \text{ k}\Omega} + \frac{V_6 - 4}{1 \text{ k}\Omega} - \frac{V_6 - 6}{1 \text{ k}\Omega} = 0$$

$$V_6 = 4 \text{ V}$$

143. [2]

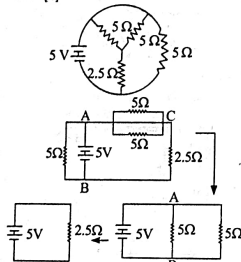



Current supplied by 5V battery

$$= 5 \text{ V} / 2.5 \Omega = 2 \text{ A}$$

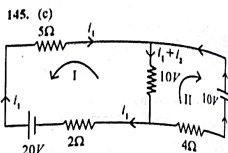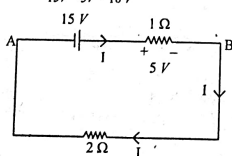144. [10] $I = \frac{15}{3} = 5 \text{ A}$

$$\therefore V_{AB} = 15 \text{ V} - 5 \times 1 \text{ V}$$

$$= 15 \text{ V} - 5 \text{ V} = 10 \text{ V}$$



Loop-I:

$$-20 + 2I_1 + 10(I_1 + I_2) + 5I_1 = 0$$

$$17I_1 + 10I_2 = 20$$

$$0 = E - Ir_2$$

$$-10 + 4I_1 + 10(I_1 + I_2) = 0$$

$$10I_1 + 14I_2 = 10$$

$$\text{Equation (i)} \times (10) - \text{Equation (ii)} \times 17$$

$$170I_1 + 100I_2 = 200$$

$$-170I_1 + 238I_2 = 170$$

$$-138I_2 = 30$$

$$I_2 = -\frac{30}{138} = -0.217 \text{ A}$$

"-ve" sign indicates that current flows from "ave" to "ve" terminal in 10V battery.

146. (a) $\epsilon - iR - iR = 0$

$$8 - 4i_1 - 4i_1 = 0, i_1 = 1 \text{ A}$$

147. (a) Let the potential at A = $V_A = 0$

Now at junction C, according to KCL, net current flow at point C is zero.

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$


$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$i_1 + i_2 = i_3 \Rightarrow 13 = 12 - i_1 = 2 - 1 = 1 \text{ A}$$

$$0.5 = 0.25 + \frac{7.5}{x}$$
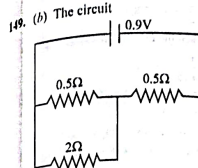
$$\frac{7.5}{x} = 0, 25; x = \frac{7.5}{0.25} = 30$$



$$\therefore R_{\text{eq}} = 0.5 + \frac{0.5 \times 2}{2 + 0.5} = \left(\frac{5}{10} + \frac{10}{25} \right) \Omega$$

$$= \frac{45}{50} = 0.9$$

$$\therefore i = \frac{0.9}{0.9} = 1 \text{ A}$$

$$i = \frac{0.9}{0.9} = 1 \text{ A}$$

$$i = \frac{0.9}{0.9} = 1 \text{ A}$$

$$i = \frac{0.9}{0.9} = 1 \text{ A}$$

$$i = \frac{0.9}{0.9} = 1 \text{ A}$$

$$S = \frac{(3 \times 10^{-3}) \cdot 10}{8 - 0.003} = 3.75 \times 10^{-3} \Omega$$

155. (c) Since all the resistance in series, Hence, $R_{\text{eq}} = 4000 \Omega$
So current passing through circuit is,


$$I = \frac{4}{4000} = \frac{1}{1000} \text{ A}$$

$$\text{Hence, } V_0 = I R = \frac{1}{1000} \times 500 = 0.5 \text{ V}$$

156. (200) Given $R_1 = 100 \text{ ohm}$

$$R_2 = 200 \text{ ohm}$$

$$V = 4 \text{ V}$$

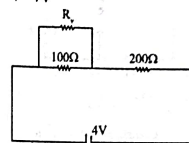

$$\frac{R_1}{R_1 + 100} = \frac{200}{3}$$

$$R_1 = 100 \Omega$$

$$\alpha = \frac{\Delta R}{R \Delta \lambda} = \frac{-0.6}{3 \times 20}$$

$$= -10^{-3} \text{ } ^\circ\text{C}^{-1}$$

$$157. (c) i = \frac{E_{\text{eq}}}{r_{\text{eq}}} = \frac{8 \times 5}{8 \times 0.2} = 25 \text{ A}$$

$$\text{As, } V_{\text{eq}} = E - ir$$

$$= 5 - 0.2 \times 25 = 0$$

$$158. (c) \text{ Let the resistor to be connected in series with } R_0 \text{ be } R.$$

$$I_g = \frac{R_0}{R_0 + R}$$

$$R = \frac{V}{I_g} - R_0 = \frac{100}{5 \times 10^{-3}} - 50$$

$$= 20000 - 50$$

$$= 19950 \Omega$$

$$159. (d) \text{ Given } G = 10 \Omega$$

$$I_g = 3 \text{ mA}$$

$$I = 8 \text{ A}$$

$$I_g = 3 \text{ mA}$$

$$I = 8 \text{ A}$$

$$I_g = 3 \text{ mA}$$

$$I = 8 \text{ A}$$

$$I_g = 3 \text{ mA}$$

$$I = 8 \text{ A}$$

$$I_g = 3 \text{ mA}$$

$$I = 8 \text{ A}$$

$$I_g = 3 \text{ mA}$$

$$I = 8 \text{ A}$$

$$I_g = 3 \text{ mA}$$

$$I = 8 \text{ A}$$

$$I_g = 3 \text{ mA}$$

$$I = 8 \text{ A}$$

$$I_g = 3 \text{ mA}$$

$$I = 8 \text{ A}$$

$$I_g = 3 \text{ mA}$$

$$I = 8 \text{ A}$$

$$I_g = 3 \text{ mA}$$

$$I = 8 \text{ A}$$

$$I_g = 3 \text{ mA}$$

$$I = 8 \text{ A}$$

Solving (i) and (ii), we get

$$r_1 = r_2 = 40 \text{ cm}$$

160. (Roman) By using,

$$I_1 S_1 = I_2 S_2$$

$$\Rightarrow \frac{95}{160} IS = \frac{5I}{100} G$$

$$\Rightarrow S = \frac{G}{19}$$

$$\Rightarrow S = \frac{G}{19}$$

$$\Rightarrow S = \frac{G}{19}$$

$$\Rightarrow S = \frac{G}{19}$$

$$\Rightarrow S = \frac{G}{19}$$

$$\Rightarrow S = \frac{G}{19}$$

$$\Rightarrow S = \frac{G}{19}$$

$$\Rightarrow S = \frac{G}{19}$$

The equivalent resistance


$$R_{eq} = \frac{10^4 R}{10^4 + R}$$

$$V = 4V, I = 2mA$$

$$I = \frac{V}{R_{eq}} = 2 \times 10^{-3} = \frac{4(10^4 + R)}{10^4 R}$$

$$= 20R = 40000 + 4R \Rightarrow R = 2500\Omega$$

166. (160)

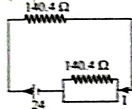

$$R_{eq} = 140.4 + \frac{240 \times 10}{240 + 10}$$

$$R_{eq} = 150 \Omega$$

$$\text{Reading of ammeter} = \frac{24}{150}$$

$$= 160 \text{ mA}$$

167. (b) Given:

$$G = 200 \Omega \text{ \& } i_1 = 20 \mu A$$

$$i = i_1 \left(\frac{G}{S} + 1 \right)$$

$$= 20 \times 10^{-6} = 20 \times 10^{-6} \left(\frac{200}{S} + 1 \right)$$

$$\Rightarrow S = 0.2 \Omega$$

168. (c) For voltmeter, Apply Kirchhoff's

law $V = (I_1 + I_2)G$

$$-I_1 R = 0$$

$$R = \frac{V}{I_1} - G$$



$$= \frac{50}{10^{-3}} - 54 = 49946$$

$$= 49946 \Omega = 50k\Omega$$

For ammeter, $I_g G - (I - I_g)R = 0$

$$r = \frac{I_g G}{I - I_g} = \frac{10^{-3} \times 54}{(10^{-3} - 1) \times 10^{-3}} = 60 \Omega$$

169. (a) Error of voltmeter decreases with increase in its resistance.

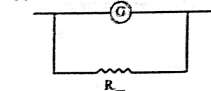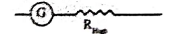170. (c) Galvanometer to Ammeter $\Rightarrow$ Galvanometer to Voltmeter $\Rightarrow$ 

171. [30]


$$\frac{R_1 + R_2}{10} = \frac{60}{40} \Rightarrow R_1 + R_2 = 15$$

$$\text{Now } \frac{R_1 R_2}{(R_1 + R_2) \times 3} = \frac{40}{60}$$

$$\Rightarrow R_1 R_2 = 30\Omega^2$$

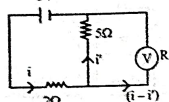172. [20]

$$i' = \frac{2V}{5\Omega} = \frac{2}{5} A$$



$$i = \frac{(3-2)}{2} = \frac{1}{2} A$$

 $\therefore$ Current through voltmeter

$$= \frac{1}{2} \times \frac{2}{5} = \frac{1}{5} A$$

 $\therefore$ For voltmeter $V = (i - i')R$


$$2 = \left(\frac{1}{5} - \frac{1}{2} \right) R \Rightarrow R = 20\Omega$$

173. [50]

Given, $I = 250 \text{ mA} = 0.250 A$

$$R_g = 5\Omega$$


$$G = ?$$

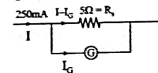

$$(I - I_g)R_g = I_g G$$

$$\Rightarrow I_g = \frac{IR_g}{R_g + G} = \frac{0.250 \times 5}{5 + G}$$

$$\frac{1050\Omega}{25V}$$

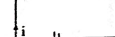

$$I_g = \frac{25}{1050 + G}$$

$$\text{From (i) and (ii)}$$

$$\frac{0.250 \times 5}{5 + G} = \frac{25}{1050 + G}$$

$$G = 50\Omega$$

174. [2] For a balanced meter - bridge,

$$\frac{R}{S} = \frac{l}{100 - l}$$

$$\Rightarrow \frac{2}{\left(\frac{3X}{1+X} \right)} = \frac{40 + 22.5}{60 - 22.5} \times \frac{5}{3}$$

$$\Rightarrow \frac{6}{5} = \frac{3X}{3+X}$$

$$\Rightarrow X = 2$$

175. [5] When the external resistance, $R = 5\Omega$

$$\frac{E}{r+S} \times 5 = 200x$$

$$\frac{E \times 15}{r+15} = 300x$$

Dividing eqn (i) by (ii)


$$\Rightarrow r = 5\Omega$$

176. (b) Given, $G = 72\Omega$, $S = 8\Omega$

$$\Rightarrow I_g G = (I - I_g)S$$

$$\Rightarrow \frac{I - I_g}{I_g} = \frac{G}{S}$$
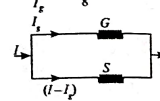
$$\Rightarrow \frac{I}{I_g} - 1 = \frac{72}{8}$$



$$\Rightarrow \frac{I}{I_g} = 10$$


$$\Rightarrow \frac{I_g}{I} = \frac{1}{10}$$

$$\Rightarrow \frac{I}{I_g} \times 100 = 10\%$$

% of current which passes through galvanometer is 10%.

177. (b) In galvanometer

$$I_g G = (I - I_g)S$$

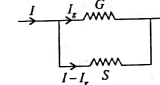

$$\frac{I_g}{I} = \frac{S}{S+G} \Rightarrow \frac{1}{3} = \frac{S}{S+G} \Rightarrow G = 2S$$

178. (b) Given, $G = 72\Omega$, $S = 8\Omega$

$$\Rightarrow I_g G = (I - I_g)S$$

$$\Rightarrow \frac{I - I_g}{I_g} = \frac{G}{S}$$


$$\Rightarrow \frac{I}{I_g} - 1 = \frac{72}{8}$$

$$\Rightarrow \frac{I}{I_g} = 10$$

$$\Rightarrow \frac{I_g}{I} = \frac{1}{10}$$

$$\Rightarrow \frac{I}{I_g} \times 100 = 10\%$$

% of current which passes through galvanometer is 10%.

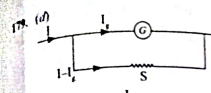Figure of merit $\frac{1}{\theta} = K$

$$I_g = K\theta$$

$$I = \frac{I_g (G + S)}{S}$$

$$\therefore I = \frac{nK}{S} (G + S)$$

$$\frac{S}{100 - I} = \frac{I}{100 - I} \Rightarrow S = 5.6 \times \frac{30}{100 - 30}$$

$$\Rightarrow S = \frac{3}{7} \times 5.6k\Omega = 3 \times 0.8k\Omega$$

$$= 2.4k\Omega = 2400\Omega$$

181. [19]

Unknown resistance R Known resistance, $P = 15\Omega$

At null point

$$\frac{P}{R} = \frac{I}{100 - I} = \frac{15}{100 - (43)}$$

$$R = 19\Omega$$

182. [40]

Since, potential gradient is independent of area therefore, balancing point will be same i.e.

$$x = 40 \text{ cm}$$

183. [10]

Using the balance condition of Wheatstone bridge:

$$\frac{R}{3} = \frac{4}{6} \Rightarrow R = 2\Omega$$

Equivalent resistance of the circuit $R_{eq} =$


$$\frac{9 \times 6}{9 + 6} = \frac{54}{15} \Omega$$

$$R_{eq} = 245\Omega$$

From ohm's law,

$$i = \frac{36}{\frac{54}{15}} = 10 A$$

184. [8]

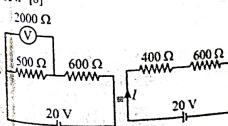

$$I = \frac{20}{400 + 600} = 20 \text{ mA}$$

Current through the voltmeter =

$$I \times \frac{500}{2500} = 20 \times \frac{500}{2500} = 4 \text{ mA}$$

 $\therefore$ Voltage across the voltmeter = Current through in voltmeter $\times$ voltmeter resistance

$$= 4 \times 10^{-3} \times 2000 = 8 V$$

185. [20]

$$\text{Initially, } \frac{P}{Q} = \frac{40}{60} = \frac{2}{3}$$

$$\frac{4}{Q} = \frac{2}{3} \Rightarrow Q = 6\Omega$$

$$\text{Finally, } \frac{P+X}{Q} = \frac{80}{20} = \frac{4}{1}$$

$$\frac{4+X}{6} = \frac{4}{1}$$

$$X = 24 - 4 = 20\Omega$$


186. (c) Current at full deflection,

$$I_m = \frac{\text{Total number of division}}{\text{Sensitivity}}$$

$$= \frac{50}{2} = 25 \text{ mA}$$

$$R = \frac{V}{I_m} = \frac{50}{25} = 2\Omega$$

187. (d)

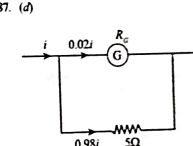

For Ammeter

$$I_0 R_G = (I - I_0)S$$

$$\frac{2I}{100} R_G = \frac{98I}{100} \times 5$$

$$R_G = 245\Omega$$

188. (c) Let, $V_A = 10 V$, $V_B = 3 V$, $V_C = 0 V$, and

$$V_D = 0 V$$

Net current from B is zero, so,

$$\frac{x-10}{100} + \frac{x-y}{15} + \frac{x-0}{60} = 0 \Rightarrow 53x - 20y = 30$$

Net current from D is zero, so,

$$\frac{y-10}{60} + \frac{y-x}{15} + \frac{y-0}{5} = 0 \Rightarrow 17y - 4x = 10$$

Solving equations (i) and (ii), we get,


$$x = 0.865 \text{ and } y = 0.792$$

$$I_0 = \frac{x-y}{15} = 4.87 \text{ mA}$$

189. [48]

Using the galvanometer coil balanced formula, under balanced condition,

$$\frac{12}{72 - x} = \frac{6}{144 - 48 \text{ cm}}$$

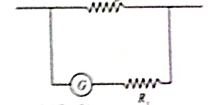190. (a) I_g is current in the galvanometer G is the resistance of the galvanometers

$$V = I_g (G + R)$$

$$1 = I_g (G + R)$$

$$2 = I_g (G + R + R_g)$$

$$2 = 1 + I_g R_g$$

$$I_g R_g = 1$$

$$R_g = G + R$$

191. (c) For parallel combination of $10 k\Omega$ and 400Ω

$$R = \frac{40000}{104} = 384.61 \Omega$$

The potential difference across 400Ω is

$$V_{400 \Omega} = \frac{384.61}{384.61 + 400} \times 6 = 1.95 V$$

192. (d) Current passing through the

galvanometer

$$I = 6 \text{ mA}$$

Deflection in galvanometers, $\theta = 2^\circ$

Figure of Merit

$$= C = \frac{I}{\theta} = \frac{6 \times 10^{-3}}{2} = 3 \times 10^{-3} \text{ A/m}^\circ$$

193. (a) Voltage in the galvanometer,

$$V_g = I_g R_g = 10^{-3} \times 100$$

$$= \frac{100}{1000} = 0.1 V$$

Potential difference, $V = 10 V$

$$= R_g \left(\frac{V}{V_g} - 1 \right)$$

$$= 100 \times 99 = 99 K\Omega$$

194. [40] $\frac{V}{2} = \frac{75}{25} = 3$, $R = \frac{50I}{2I}$

$$R = \frac{40 \left(\frac{1}{2} \right)}{\pi \left(\frac{1}{2} \right)} = 2R$$

$$\text{then } \frac{V}{R} = \left(\frac{100 - I}{2R} \right)$$

$$\frac{100 - I}{I} = \frac{X}{2R} = \frac{3}{2}$$

$$I = 40.00 \text{ cm}$$

capacitor, therefore $I = \frac{3}{6+4} = \frac{3}{10}$

Potential difference on 6Ω resistance

$$V = 6 \times \frac{3}{10} = 1.8 \text{ volt}$$

Capacitor will have same potential difference there fore, charge on it $q = CV = (4 \mu F) \cdot (1.8 \text{ volt}) = 7.2 \mu C$.

220. (b) At steady state, capacitors are open.

$$\therefore i = \frac{4V}{6+2+8} = \frac{1}{4} A$$

Voltage across C_1 is

$$V_1 = V_{AC} = i(6\Omega + 2\Omega) = 8i \text{ Volt}$$

Voltage across C_2 is

$$V_2 = V_{BD} = i(2\Omega + 8\Omega) = 10i \text{ Volt}$$

$$\Rightarrow \frac{V_1}{V_2} = \frac{8i}{10i} = \frac{4}{5}$$

221. (d) $q = q_0 e^{-t/RC}$
(discharging eq. of capacitor)

$$t \rightarrow \frac{t}{2} \Rightarrow q \rightarrow \frac{q_0}{\sqrt{2}}$$

$$\frac{q_0}{\sqrt{2}} = q_0 e^{-t_1/\tau}$$

$$\sqrt{2} = e^{-t_1/\tau} \Rightarrow t_1 = \tau \ln \sqrt{2}$$

$$\frac{q_0}{8} = q_0 e^{-t_2/RC}$$

$$8 = e^{t_2/RC} \Rightarrow t_2 = \tau \ln 8$$

$$\frac{t_1}{t_2} = \frac{\ln \sqrt{2}}{\ln 8} = \frac{\frac{1}{2} \ln 2}{3 \ln 2} = \frac{1}{6}$$

222. [10]

$$q = CV$$

$$= \left(\frac{11}{10} \times 10^{-6} \right) \left(\frac{100}{11} \right)$$

$$= 10 \mu C$$

223. (b) $V = V_0(1 - e^{-t/RC})$

$$V = 10(1 - e^{-t/RC})$$

$$2 = 10(1 - e^{-t/RC})$$

$$\frac{1}{10} = 1 - e^{-t/RC}$$

$$e^{-t/RC} = \frac{10}{9}$$

$$\frac{t}{RC} = \ln \left(\frac{10}{9} \right) = 0.105$$

$$C = \frac{10^{-6}}{10 \times 0.105} = 0.95 \mu F$$

224. [100]

We know that, charge on the capacitor, $Q = CV$

$$Q = 50 \mu F \times 2V = 100 \times 10^{-6} C$$

$$Q = 100 \mu C$$

Hence, charge on the upper plate of capacitor is $100 \mu C$

225. (d) Given, $C = 1 \mu F = 1 \times 10^{-6} F$

$$V_0 = 100 \text{ volt}, V = 50 \text{ volt}$$

$$R = 100 \Omega$$

$$\text{Where } \tau = RC = 100 \times 10^{-6} \text{ sec}$$

$$50V = 100V \left(1 - e^{-t/10^{-4}} \right)$$

$$\frac{1}{2} = 1 - e^{-10^4 t} \Rightarrow \frac{1}{2} = e^{-10^4 t}$$


$$2 = e + 104t \Rightarrow \ln 2 = 104t$$

$$t = \frac{\ln 2}{10^4}$$

$$t = 0.693 \times 10^{-4} \text{ sec.}$$

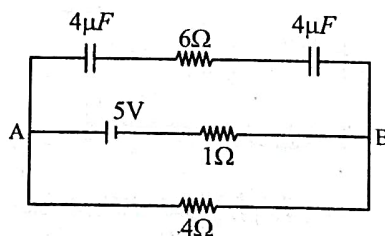226. (d) $V_{AB} = \frac{5}{5} \times 4 = 4V$

$$\Rightarrow Q = Ceq V = 2 \times 4 = 8 \mu C [\because Ceq = 2 + 2 = 4 \mu F]$$




227. [2] $I = \frac{V}{R} = \frac{30/3}{5 \times 10^6} = 2 \times 10^{-6}$

228. (a) $\tau = RC = 10 \mu s$

For $0 < t < 5 \mu s$, it will get charged. For $5 < t < 10 \mu s$ potential is constant and again gets charged after that.

229. [8]

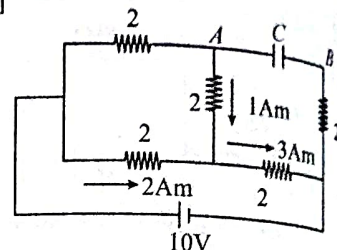

After solving the circuit we got the final current distribution as shown in the above diagram. So potential difference between A and B is

$$0 + (2 \times 3) + (2 \times 1) = 8 \text{ volt}$$

230. [6] After connection is common potential

$$V_{\text{common}} = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2} = \frac{60 \times 20 + 0}{120} = 10V$$

Energy loss =

$$U_i - U_f = \frac{1}{2} CV^2 - \frac{1}{2} (2C) \times V_{\text{Common}}^2$$


$$= \frac{1}{2} \times 60 \times 10^{-12} \times (20)^2$$

$$- 60 \times 10^{-12} \times (10)^2$$


$$= 60 \times 10^{-12} (200 - 100)$$

$$= 6000 \times 10^{-12}$$

$$= 6 \text{ nJ}$$

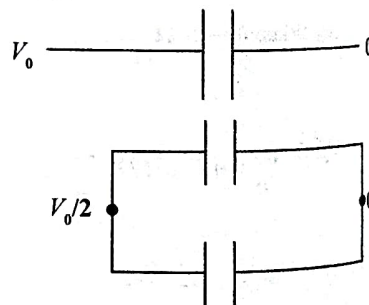

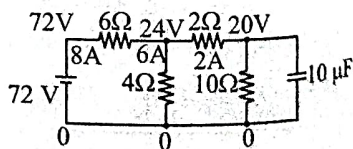231. (a) Different potential is shown at different points.



$$VC = 20 \text{ V}, C = 10 \mu F$$

$$\therefore q = CV = 10 \times 10^{-6} \times 20$$

$$q = 200 \mu C$$